COL216 Lab Assignment-2 (S1)

- Mayank Mangla (2020CS50430)

1 Introduction

The aim of this project is to design hardware for implementing a processor that can execute a subset of ARM instructions described below. Starting with a skeleton design, the hardware is built in several stages, adding some functionality at every stage. The designs are to be expressed in VHDL and then simulated and synthesized.

Stage 1: This stage is designing and testing the basic modules of the processor. The module set includes ALU, Register File, Program Memory and Data Memory.

The report for the stage 1 is given below:

2 Program Information

This program has been test on "eda playground" using "-2019 -o" flags.

The program is in four parts or modules: ALU (arithmetic and logic unit), Register File, Program Memory and Data Memory. Each module consists of 3 files. One for design, one for test bench and one for run.do.

All the files have some same part of the code:

```
library IEEE;
use IEEE.numeric_std.all;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

These are the header files that are used in the program. Other than this, each file has an entity declaration and its architecture implementation.

Run.do file has a common code that is the command to synthesis the module.

```
setup_design -manufacturer Xilinx -family Artix-7 -part 7A100TCSG324
foreach arg $::argv {
   add_input_file $arg
}
compile
synthesize
auto_write precision.v
report_output_file_list
report_area
report_timing
#exec cat precision.v
```

Next is the module wise understanding of the code:

2.1 ALU

This module does all the data processing instructions. This module responds to 16 different instructions.

The inputs to this are:

- 1. two operand, each 32 bit unsigned integer
- 2. 4 bit instruction
- 3. carry in (single bit)

The outputs are:

- 1. carry out (single bit)
- 2. result of the instruction on the two input operands giving 32 bit unsigned integer

The different instructions have different 4 bit standard op code that is followed by the arm instruction set. Accordingly we perform the operation on the operands.


```
architecture implement_alu of ALU is
begin
    process(op1,op2,cin,opc)
                                                          -- triggered by the change in inputs
    variable temp: std_logic_vector(32 downto 0); -- temporary variables
    variable tempbit: std_logic := '0';
                                                          -- defined for sequential statements
    begin
        case(opc) is
                                                          -- case switches for operations
            when "0000" \Rightarrow temp := (tempbit & op1) and (tempbit & op2);
            when "0001" => temp := (tempbit & op1) xor (tempbit & op2);
            when "0010" => temp := (tempbit & op1) + (not (tempbit & op2)) + 1;
            when "0011" => temp := (tempbit & op2) + (not (tempbit & op1)) + 1;
            when "0100" => temp := (tempbit & op1) + (tempbit & op2);
            when "0101" => temp := (tempbit & op1) + (tempbit & op2) + cin;
            when "0110" \Rightarrow temp := (tempbit & op1) + (not (tempbit & op2)) + cin;
            when "0111" \Rightarrow temp := (tempbit & op2) + (not (tempbit & op1)) + cin;
            when "1000" \Rightarrow temp := (tempbit & op1) and (tempbit & op2);
            when "1001" => temp := (tempbit & op1) xor (tempbit & op2);
            when "1010" \Rightarrow temp := (tempbit & op1) + (not (tempbit & op2)) + 1;
            when "1011" => temp := (tempbit & op1) + (tempbit & op2);
            when "1100" => temp := (tempbit & op1) or (tempbit & op2);
            when "1101" => temp := tempbit & op2;
            when "1110" => temp := (tempbit & op1) and (not (tempbit & op2));
            when "1111" => temp := (not (tempbit & op2));
            when others => temp := "ZZZZZZZZZZZZZZZZZZZZZZZZZZZZZZ;;
        end case;
        result <= temp(31 downto 0);</pre>
                                                              -- updating the result
                                                              -- and carry out
        cout \leq temp(32);
    end process;
                                                              -- ending process
                                                              -- ending implementation
end implement_alu;
```

Now the test bench for the ALU module test the design for different inputs which are hard coded in the test bench code. Its code can be displayed as (excluding something that is very trivial)


```
process
```

```
-- input 2
opc_in <= "1111";
c1_in <= '1';
-- loop checking for all opcodes
for I in 0 to 15 loop
   v := opc_in;
   opc_in <= v + "0001";
   wait for 10 ns;
end loop;
wait for 10 ns;
-- input 3
a_in <= "10101010101010101010101010101010";</pre>
b_in <= "111111111111111111100000000000000000";</pre>
c1_in <= '1'; opc_in <= "1111";
-- loop checking for all opcodes
for I in 0 to 15 loop
   v := opc_in;
   opc_in <= v + "0001";
   wait for 10 ns;
end loop;
wait for 10 ns;
wait;
end process;
```

 The output signal to these test case are:



 Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



The logs of the synthesis of ALU module are provided here:

```
# Info: Device Utilization for 7A100TCSG324
# Info: Resource
                        Used
                            Avail
                                 Utilization
# Info: -----
# Info: IOs
                        102
                            210
                                 48.57%
                            32
                                  0.00%
# Info: Global Buffers
                        0
# Info: LUTs
                                  0.21%
                        133
                            63400
```

```
# Info: CLB Slices
                            32
                                 15850
                                        0.20%
                            0
                                        0.00%
# Info: Dffs or Latches
                                 126800
# Info: Block RAMs
                            0
                                 135
                                        0.00%
# Info: DSP48E1s
                            0
                                 240
                                        0.00%
# Info: -----
# Info: Library: work Cell: ALU View: implement_alu
# Info: Number of ports:
                                  102
                                  369
# Info: Number of nets:
# Info: Number of instances :
                                  300
# Info: Number of references to this view :
                                    0
# Info: Total accumulated area:
# Info: Number of LUTs :
                                  133
# Info: Number of LUTs with LUTNM/HLUTNM:
                                    4
# Info: Number of MUX CARRYs :
                                   32
# Info: Number of accumulated instances :
                                  300
```

2.2 Register File

This module contains all the registers' addresses. This module enables us to read and write data from or to registers.

The inputs to this are:

- 1. two addresses of the register of which the data is to be read, each 4 bit unsigned integer
- 2. one address of the register which is to be overwritten, each 4 bit unsigned integer
- 3. clock and write enable (single bit)

The outputs are:

1. two data vectors that have been read from the two addresses (32 bit each)


Here we have a memory data type that is an array of length 16 each element is of 32 bit. It stores the registers data. Then we read the data ignoring the condition of the clock. Then on the rising edge of the clock we write the data on the memory


```
architecture implement_rf of RegisterFile is
    type mem is array (0 to 15) of std_logic_vector(31 downto 0);
    -- defining a type that is array of 16 std_logic_vector (32 bits)
    signal memory: mem;
                                                     -- internal signal that is of mem type
begin
    dout1 <= memory(conv_integer(rad1));</pre>
                                                     -- reading the register and outputing the same
    dout2 <= memory(conv_integer(rad2));</pre>
                                                     -- without any intervention of clock
    process(clk)
                                                     -- process when clock or writing is triggered
    begin
        if (rising_edge(clk)) then
                                                     -- at rising edge of the clock
            if wen = '1' then
                                                     -- and write enable set
                memory(conv_integer(wad)) <= data; -- write the data to the register address
            end if;
        end if;
    end process;
                                                      -- end process
end implement_rf;
                                                     -- end implementation
```

Now the test bench for the Register File module test the design for different inputs which are hard coded in the test bench code. First we write some values in the register and then read them. Its code can be displayed as (excluding something that is very trivial)

process begin clock <= '1'; r1 <= "0000"; r2 <= "1000"; $W \le "0000"$; we <= '1'; -- write in memory for a in 0 to 15 loop clock <= not clock;</pre> wait for 5 ns; $w \le w + 1;$ $d \le d + 2;$ clock <= not clock;</pre> wait for 5 ns; -- rising edge of the clock end loop; we <= '0'; -- read from memory for b in 0 to 7 loop clock <= not clock;</pre> wait for 5 ns; r1 <= r1 + 1; $r2 \le r2 + 1;$ wait for 5 ns; -- rising edge of the clock clock <= not clock;</pre> end loop; wait; end process;

 The output signal to these test case are:



 

The logs of the synthesis of Register File module are provided here:

```
# Info: Device Utilization for 7A100TCSG324
# Info: Resource
                          Used
                              Avail
                                  Utilization
# Info: -----
# Info: IOs
                               210
                          110
                                    52.38%
# Info: Global Buffers
                                     3.12%
                          1
                               32
# Info: LUTs
                          48
                               63400
                                     0.08%
# Info: CLB Slices
                          12
                               15850
                                     0.08%
# Info: Dffs or Latches
                          0
                               126800
                                     0.00%
# Info: Block RAMs
                          0
                               135
                                     0.00%
# Info: Distributed RAMs
# Info:
      RAM32M
                          10
# Info:
      RAM64M
                          2
# Info: DSP48E1s
                          0
                               240
                                     0.00%
# Info: ------
# Info: Library: work Cell: RegisterFile
                             View: implement_rf
# Info: Number of ports:
                                110
# Info: Number of nets:
                                220
# Info: Number of instances :
                                111
# Info: Number of references to this view :
                                 0
# Info: Total accumulated area:
# Info: Number of LUTs:
                                48
# Info: Number of accumulated instances:
                                123
```

2.3 Program Memory

This module contains all the instructions stored in the form of 32 bit number each. We read the data from the this module and perform the instruction that is read. This is Read Only Memory and hence there is no port for writing into this memory.

The inputs to this are:

1. one address of the register of which the data is to be read (4 bit unsigned integer)

The outputs are:

1. one data vector that has been read from the addresses (32 bit vector)


Here we have a memory data type that is an array of length 64 each element is of 32 bits (This memory s hard coded in the code, can be modified according to the testing by changing its initialization in the code).

```
architecture implement_pm of ProgramMemory is
  type mem is array (0 to 63) of std_logic_vector(31 downto 0);
  -- mem is array of instruction in program memory
  signal memory: mem:=
  -- signal that is accessing the instruction array
  ...);
begin
  process(radd)
                          -- process on read address
  begin
    dout <= memory(conv_integer(radd));</pre>
                          -- getting the data at the given address
  end process;
end implement_pm;
```


Now the test bench for the Program Memory module test the design for different inputs which are hard coded in the test bench code. We read the instruction codes that have been coded in the program. Its code can be displayed as (excluding something that is very trivial)

```
process
begin
    -- reading the data initialized
    readaddress <= "0000000";
    for a in 0 to 63 loop
        wait for 10 ns;
        readaddress <= readaddress + "000001";
    end loop;
    wait;
end process;</pre>
```

 The output signal to these test case are:



 Note: To revert to EPWave opening in a new browser window, set that option on your user page.



age.



The logs of the synthesis of Program memory module are provided here:

```
# Info: Device Utilization for 7A100TCSG324
# Info: Resource
                     Used
                         Avail Utilization
# Info: -----
# Info: IOs
                     38
                         210
                             18.10%
# Info: Global Buffers
                     0
                         32
                              0.00%
# Info: LUTs
                     4
                         63400
                              0.01%
# Info: CLB Slices
                     0
                         15850
                              0.00%
# Info: Dffs or Latches
                     0
                         126800
                              0.00%
# Info: Block RAMs
                     0
                         135
                              0.00%
# Info: DSP48E1s
                     0
                         240
                              0.00%
# Info: -----
# Info: Number of ports :
                           38
# Info: Number of nets:
                           49
# Info: Number of instances :
                           43
# Info: Number of references to this view :
# Info: Total accumulated area:
# Info: Number of LUTs :
# Info: Number of LUTs with LUTNM/HLUTNM:
# Info: Number of accumulated instances:
                           43
```

2.4 Data Memory

This module stores the data. This is different from program memory in a way that the data in data memory can be overwritten. This has one read and one write port.

The inputs to this are:

- 1. data that is to be written, 32 bit vector
- 2. address where the data is to be written and read, 6 bit unsigned number
- 3. clock (single bit)
- 4. a 4 bit write enable

The outputs are:

1. data that is being read, 32 bit vector

The different enables have different 4 bit code which is used to write in the memory to any one byte, half word or full word. Accordingly we write to the memory.

```
architecture implement_dm of DataMemory is
    type mem is array (0 to 63) of std_logic_vector(31 downto 0); -- mem array of data
    signal memory: mem;
                                                        -- signal for the data in data memory
begin
   process(clk)
                                                        -- process with change in clock
    begin
       if(rising_edge(clk)) then
       -- if the rising edge of the clock then we do as write enables
           if wen= "0001" then memory(conv_integer(add))(7 downto 0) <= data(7 downto 0);
           elsif wen="0010" then memory(conv_integer(add))(15 downto 8) <= data(7 downto 0);
           elsif wen="0100" then memory(conv_integer(add))(23 downto 16) <= data(7 downto 0);</pre>
           elsif wen="1000" then memory(conv_integer(add))(31 downto 24) <= data(7 downto 0);
           elsif wen = "0011" then memory(conv_integer(add))(15 downto 0) <= data(15 downto 0);</pre>
           elsif wen = "1100" then memory(conv_integer(add))(31 downto 16) <= data(15 downto 0);
           elsif wen = "1111" then memory(conv_integer(add)) <= data ;</pre>
           end if;
       end if;
    end process;
    dout <= memory(conv_integer(add));</pre>
                                                       -- read the data at given index
end implement_dm;
Now the test bench for the Data Memory module test the design for different inputs which are hard
coded in the test bench code. Its code can be displayed as (excluding something that is very trivial)
process
begin
    clock <= '1'; address <= "000000";
    wenable <= "0001"; -- write a byte in memory in left most byte
    for a in 0 to 15 loop
       clock <= not clock;</pre>
                              wait for 5 ns;
       address <= address + "000001";
       wait for 5 ns; -- rising edge of the clock
       clock <= not clock;</pre>
    end loop;
    wenable <= "0010"; address <= "000000";
    -- write a byte in memory in second least significant byte
    for a in 0 to 15 loop
       clock <= not clock;</pre>
                              wait for 5 ns;
       address <= address + "000001";
       wait for 5 ns; -- rising edge of the clock
       clock <= not clock;</pre>
    wenable <= "0100"; address <= "000000";
    -- write a byte in memory in second most significant byte
    for a in 0 to 15 loop
       clock <= not clock;</pre>
                             wait for 5 ns;
       address <= address + "000001";
       clock <= not clock;</pre>
                              wait for 5 ns; -- rising edge of the clock
    end loop;
    wenable <= "1000"; address <= "000000";
    -- write a byte in memory in most significant byte
    for a in 0 to 15 loop
       clock <= not clock;</pre>
                             wait for 5 ns;
       address <= address + "000001";
       clock <= not clock;</pre>
                            wait for 5 ns; -- rising edge of the clock
```

```
end loop;
          wenable <= "0011"; -- write a byte in memory in half word (least significant)
          for a in 0 to 15 loop
                                                                                   wait for 5 ns;
                    clock <= not clock;</pre>
                    address <= address + "000001";
                    clock <= not clock;</pre>
                                                                                      wait for 5 ns; -- rising edge of the clock
          end loop;
          wenable <= "1100"; address <= "010000";</pre>
          -- write a byte in memory in half word (most significant)
          for a in 0 to 15 loop
                    clock <= not clock;</pre>
                                                                                   wait for 5 ns;
                    address <= address + "000001";
                    wait for 5 ns; -- rising edge of the clock
                    clock <= not clock;</pre>
          end loop;
          wenable <= "1111"; -- write a byte in memory in word
          for a in 0 to 15 loop
                    clock <= not clock;</pre>
                                                                                   wait for 5 ns;
                    address <= address + "000001";
                    clock <= not clock; wait for 5 ns; -- rising edge of the clock</pre>
          end loop;
          wait;
end process;
The output signal to these test case are:

        From:
        0ps
        To:
        1,120,000ps

        Get Signals
        Radix ▼
        Q
        Q
        1000%
        ◀
        ❤
        ✔
        X

                                                            SONNE 
                                     To: 1,120,000ps
 XXXX_XXXX XXXX_XXI6
                                                            To: 1,120,000ps
  XXXX_XX02 XXXX_2202
```



Note: To revert to EPWave opening in a new browser window, set that option on your user page



Note: To revert to EPWave opening in a new browser window, set that option on your user page



Note: To revert to EPWave opening in a new browser window, set that option on your user page



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.



The logs of the synthesis of data Memory module are provided here:

```
# Info: Device Utilization for 7A100TCSG324
Used Avail Utilization
# Info: Resource
# Info: -----
# Info: IOs
                      75
                          210
                              35.71%
# Info: Global Buffers
                          32
                      1
                               3.12%
# Info: LUTs
                      62
                          63400
                               0.10%
# Info: CLB Slices
                      13
                          15850
                               0.08%
# Info: Dffs or Latches
                      0
                          126800
                              0.00%
# Info: Block RAMs
                      0
                          135
                               0.00%
# Info: Distributed RAMs
                      32
# Info:
     RAM64X1S
# Info: DSP48E1s
                      0
                          240
                               0.00%
# Info: -----
# Info: Library: work Cell: DataMemory View: implement_dm
# Info: Number of ports :
                            75
# Info: Number of nets:
                           180
```

3 Conclusion

The program has been tested on different inputs and the results have been attached in the report. The submission file (.zip) contains 9 files other than this report file.

Two files each for each module. One contains the design (e.g. alu_design.vhd) and other contains the test bench for the module (e.g. alu_testbench.vhd). And one is run.do file that has been used to synthesis.